

Please check that this question paper contains 09 questions and 02 printed pages within first ten minutes.

[Total No. of Questions: 09]

[Total No. of Pages: 02]

Uni. Roll No. ....

Program: B.Tech. (Batch 2018 onward)

Semester: 4

Name of Subject: **Power Electronics**

Subject Code: **PCEE-107**

Paper ID: **16188**

Scientific calculator is Allowed

**Time Allowed: 03 Hours**

**Max. Marks: 60**

**NOTE:**

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

**Part – A**

**[Marks: 02 each]**

**Q1.**

- a) Define latching and holding current.
- b) Why freewheeling diode is used in phase controlled rectifier circuits?
- c) What did you understand by term commutation?
- d) State the purpose of Gate in SCR.
- e) How can the output frequency of a cycloconverter be changed?
- f) Why freewheeling diode is used in phase controlled rectifier circuits?

**Part – B**

**[Marks: 04 each]**

- Q2. Enumerate the various mechanisms by which thyristors can be triggered into conduction.
- Q3. Describe impulse commutation technique with required wave-shapes.
- Q4. Explain various techniques for reduction of harmonics in the inverter output voltage.
- Q5. Discuss the main types of dc choppers. Which of these is more commonly employed and why?
- Q6. Discuss the working of single phase full bridge inverter.
- Q7. Explain various control strategies used for chopper.

## Part – C

[Marks: 12 each]

- Q8. Explain the operation of dual converter with non-circulating current mode. Discuss its operation with the help of voltage waveforms across each converter. Take  $\alpha_1 = 30^\circ$ .

OR

Explain switching (dynamic/ turn off-on) characteristics of SCR.

- Q9. For a single phase one-pulse SCR controlled converter system, sketch waveforms for load voltage and load current for:

- I. RL Load
- II. RL Load with freewheeling diode across RL

From a comparison of these waveforms, discuss the advantages of using a freewheeling diode.

OR

A single phase to single phase mid-point cycloconverter is delivering power to resistive load. The supply transformer has turn ratio of 1:1:1. The frequency ratio is  $f_o/f_s = 1/3$ . The firing angle delay for all the four SCRs are the same. Sketch the time variations of the following waveforms for  $\alpha = 30^\circ$ .

- a) Supply voltage
- b) Output current and supply current.

\*\*\*\*\*